

ELECTRONICS LAB (NEC-459) LAB TEST 1

Question 1:- A resistor R is placed parallel to a Ge tunnel diode. The tunnel diode has

$$\left. \frac{di_d}{dv} \right|_{max} = \frac{1}{10} \text{ mho}$$

Find the value of R so that the combination does not exhibit negative resistance region in Volt-ampere characteristics.

Question 2:- The Zener diode can be used to prevent overloading of sensitive meter movement without affecting meter linearity. The circuit shown represent a DC voltmeter which read 20V full scale.

The meter resistance is 500 Ohm and $R_1 + R_2 = 99.5 \text{ K-Ohm}$. If the diode is 16V Zener, find R_1 & R_2 so that when $V_i > 20\text{V}$ the zener diode without conduct and overload current is shunted away from the meter.

Question 3:- Over what range of input voltage will the zener regulator circuit maintain 30V across 2K-Ohm resistor, assuming $R_s = 200\text{K-Ohm}$ and maintain zener current is 25mA.

Question 4:- Differentiate between Avalanche, Zener & Thermal breakdown.

Question 5:- (a) Tunnel diode exhibit _____ characteristics.

(b) Varactor diode are operate in _____ and their _____ capacitance varies with voltage.

(c) Zener diode operate in _____ bias for _____.

ELECTRONICS LAB (NEC-459) LAB TEST 1

Question 1:- A resistor R is placed parallel to a Ge tunnel diode. The tunnel diode has

$$\left. \frac{di_d}{dv} \right|_{max} = \frac{1}{10} \text{ mho}$$

Find the value of R so that the combination does not exhibit negative resistance region in Volt-ampere characteristics.

Question 2:- The Zener diode can be used to prevent overloading of sensitive meter movement without affecting meter linearity. The circuit shown represent a DC voltmeter which read 20V full scale.

The meter resistance is 500 Ohm and $R_1 + R_2 = 99.5 \text{ K-Ohm}$. If the diode is 16V Zener, find R_1 & R_2 so that when $V_i > 20\text{V}$ the zener diode without conduct and overload current is shunted away from the meter.

Question 3:- Over what range of input voltage will the zener regulator circuit maintain 30V across 2K-Ohm resistor, assuming $R_s = 200\text{K-Ohm}$ and maintain zener current is 25mA.

Question 4:- Differentiate between Avalanche, Zener & Thermal breakdown.

Question 5:- (a) Tunnel diode exhibit _____ characteristics.

(b) Varactor diode are operate in _____ and their _____ capacitance varies with voltage.

(c) Zener diode operate in _____ bias for _____.